

Modified Single-Cycle MIPS Architecture with DSP Unit

Presented by: Mohaned Asker, Mohamed Alaa, Marcelino
Emad, Sara Abdelnasser, Hana Nasef




What is a Single-Cycle Processor?

A Single-Cycle CPU completes each instruction in exactly one clock cycle.

Features:

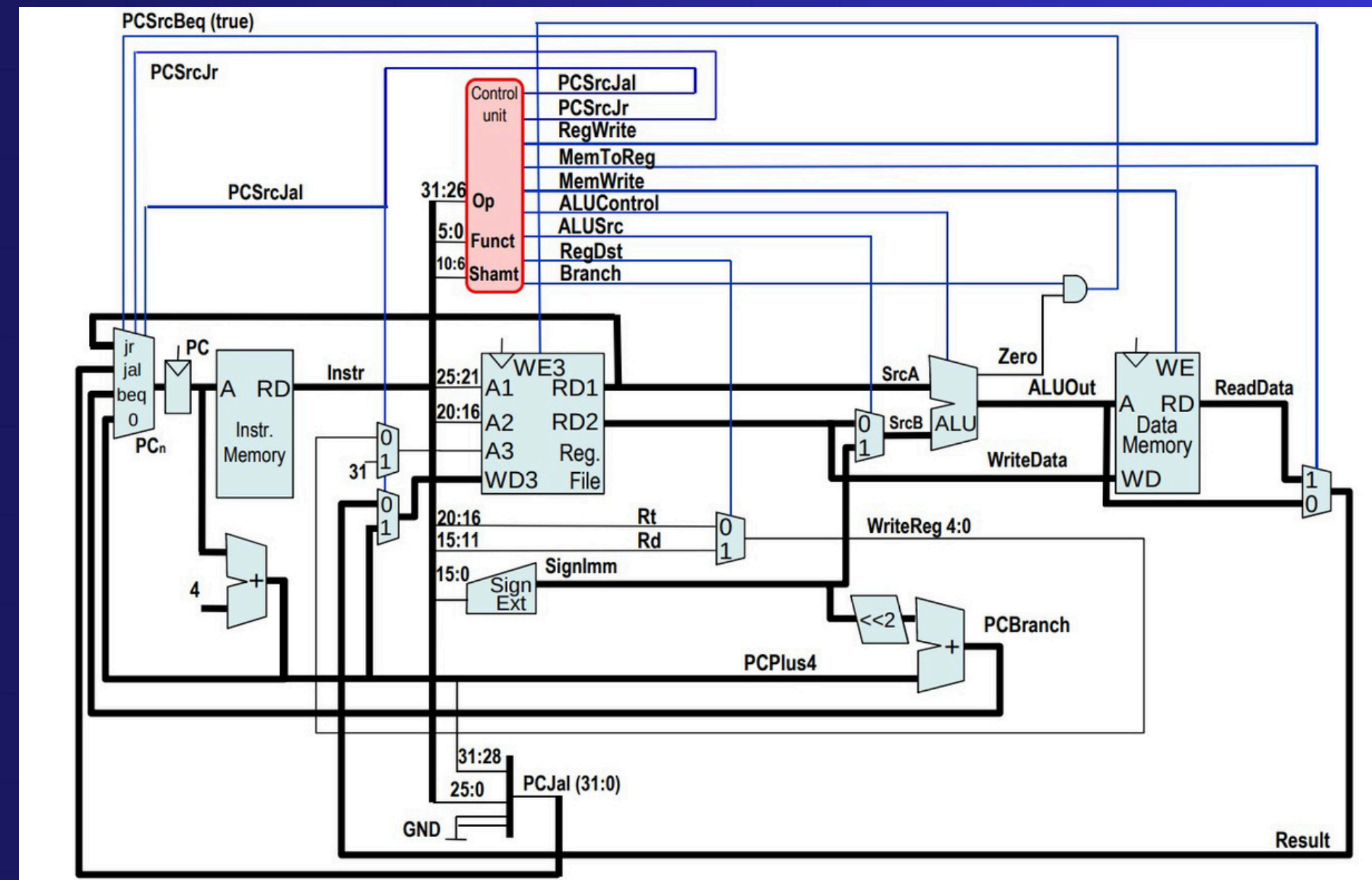- One instruction = one clock cycle.
- Simple design.
- Long clock cycle (to accommodate slowest instruction).
- Easier to understand and implement.



What is DSP (Digital Signal Processing)?

Digital Signal Processing is the use of mathematical operations to manipulate signals (like audio, images, or sensor data) in digital form.


A DSP unit is a specialized hardware block inside a processor that:

Performs operations like:

- Filtering (FIR, IIR)
- Convolution
- FFT (Fourier transform)
- Multiply-Accumulate (MAC)


Why DSP?

- Real-time signal handling
- Reduces CPU load
- Improves performance

 


Phase 1 – Standard MIPS CPU Implementation


1. Datapath:

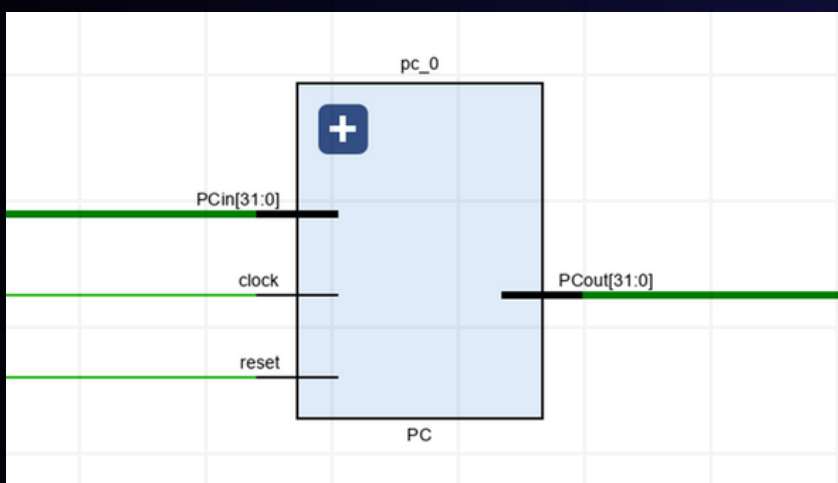


PC

 


Shift Left 2

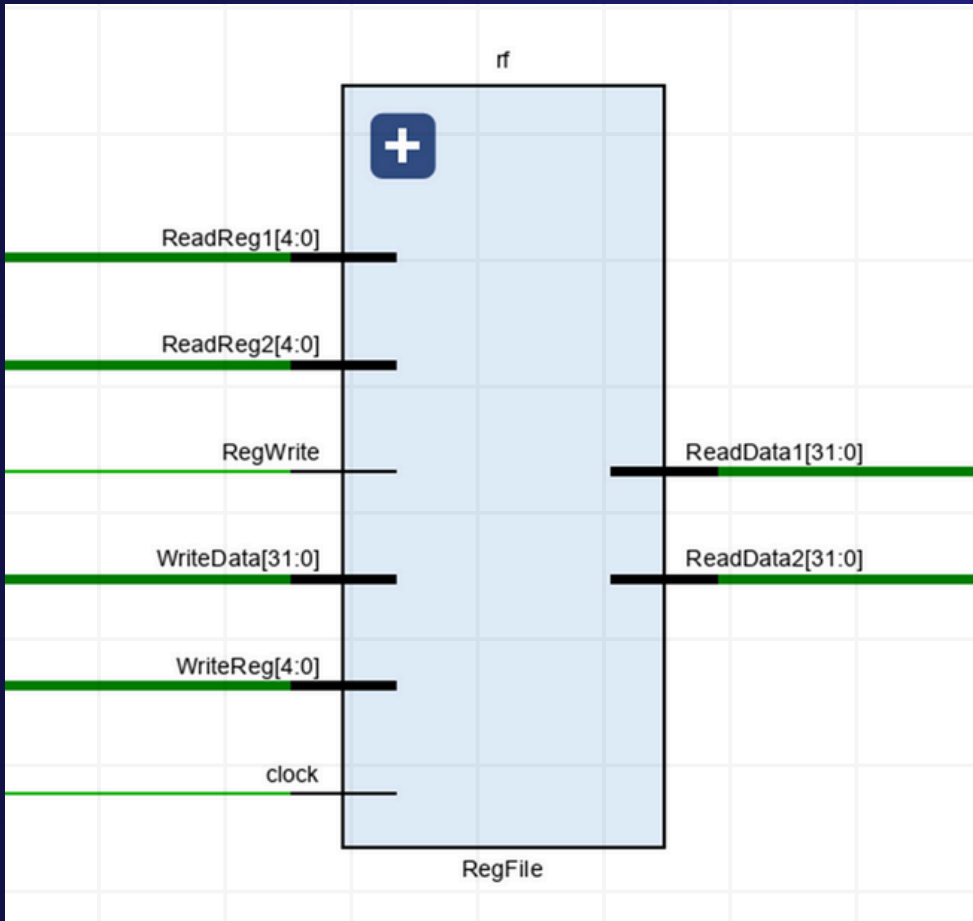


Register File

 


Sign Extend

 

Adder

 


Multiplexer

 

ALU

Phase 1 – Standard MIPS CPU Implementation

2. Control Unit:

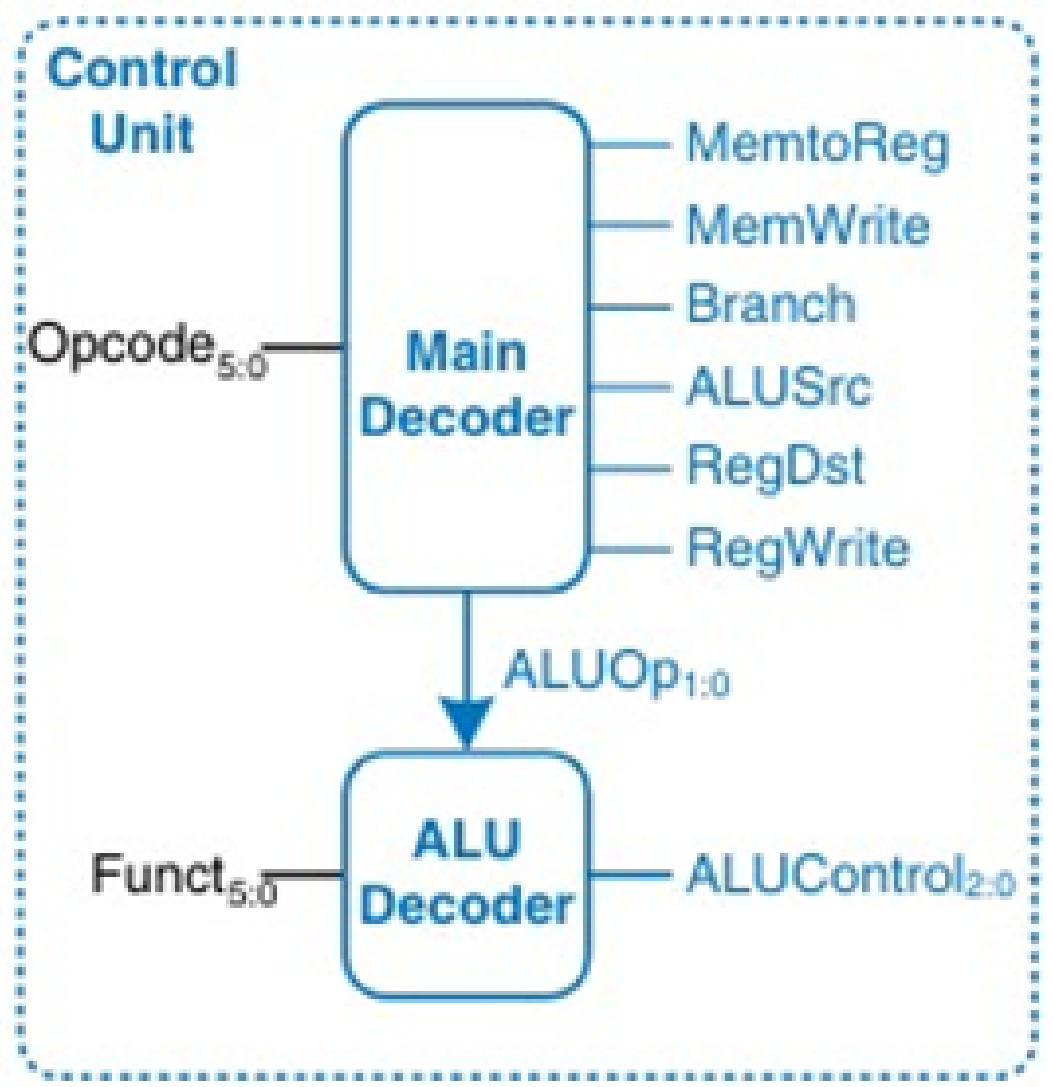

MIPS Control Unit


Instruction	Opcode	RegWrite	RegDst	ALUSrc	Branch	MemWrite	MemtoReg	ALUOp	Jump
R-type	0	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	0	0
sw	101011	0	X	1	0	1	X	0	0
beq	100	0	X	0	1	0	X	1	0
addi	1000	1	0	1	0	0	0	0	0
j	10	0	X	X	X	0	X	XX	1

Main Decoder's Truth Table

Op	Funct	ALUControl
0	XXXXXX	010 (add)
1	XXXXXX	110 (sub)
1X	100000	010 (add)
1X	100010	110 (sub)
1X	100100	000 (and)
1X	100101	001 (or)
1X	101010	111 (slt)

ALU Decoder

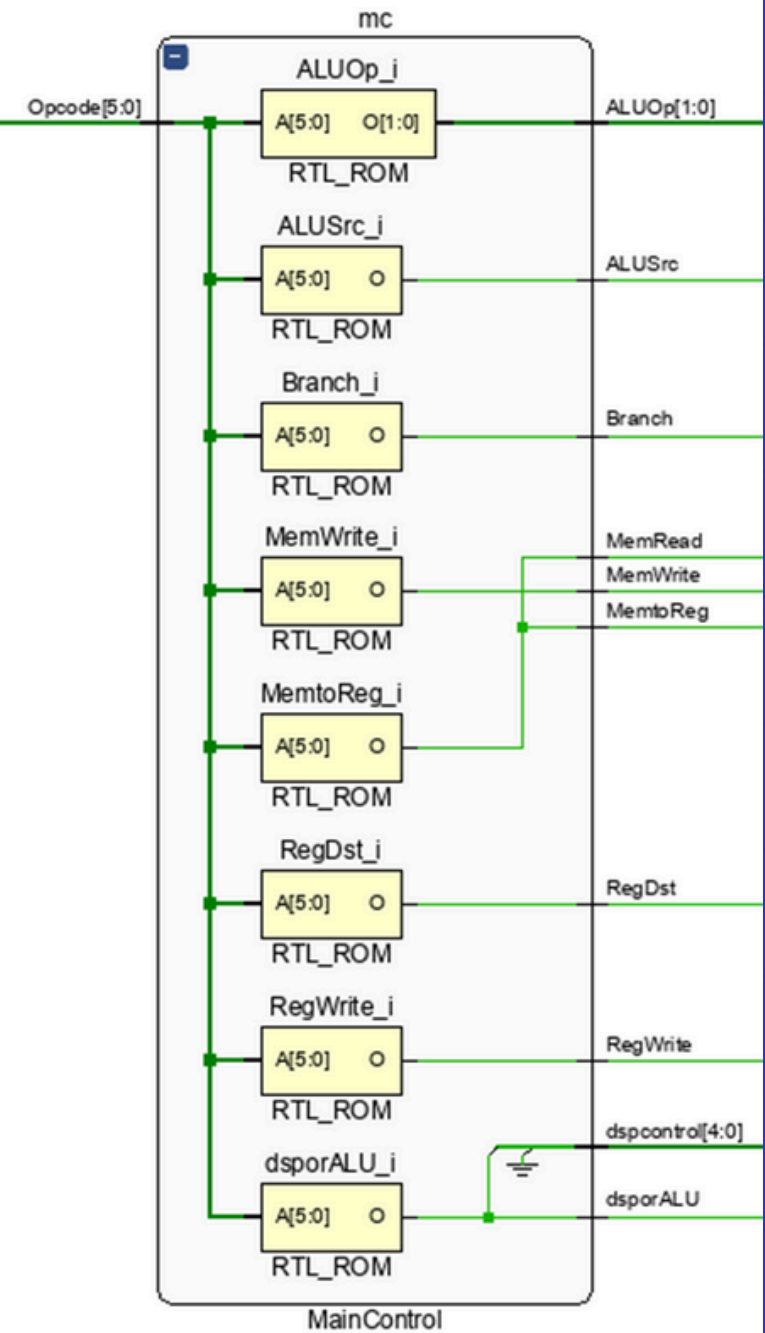
After implementing the main decoder and the ALU decoder




Control Unit

Phase 1 – Standard MIPS CPU Implementation

3. External Memory:

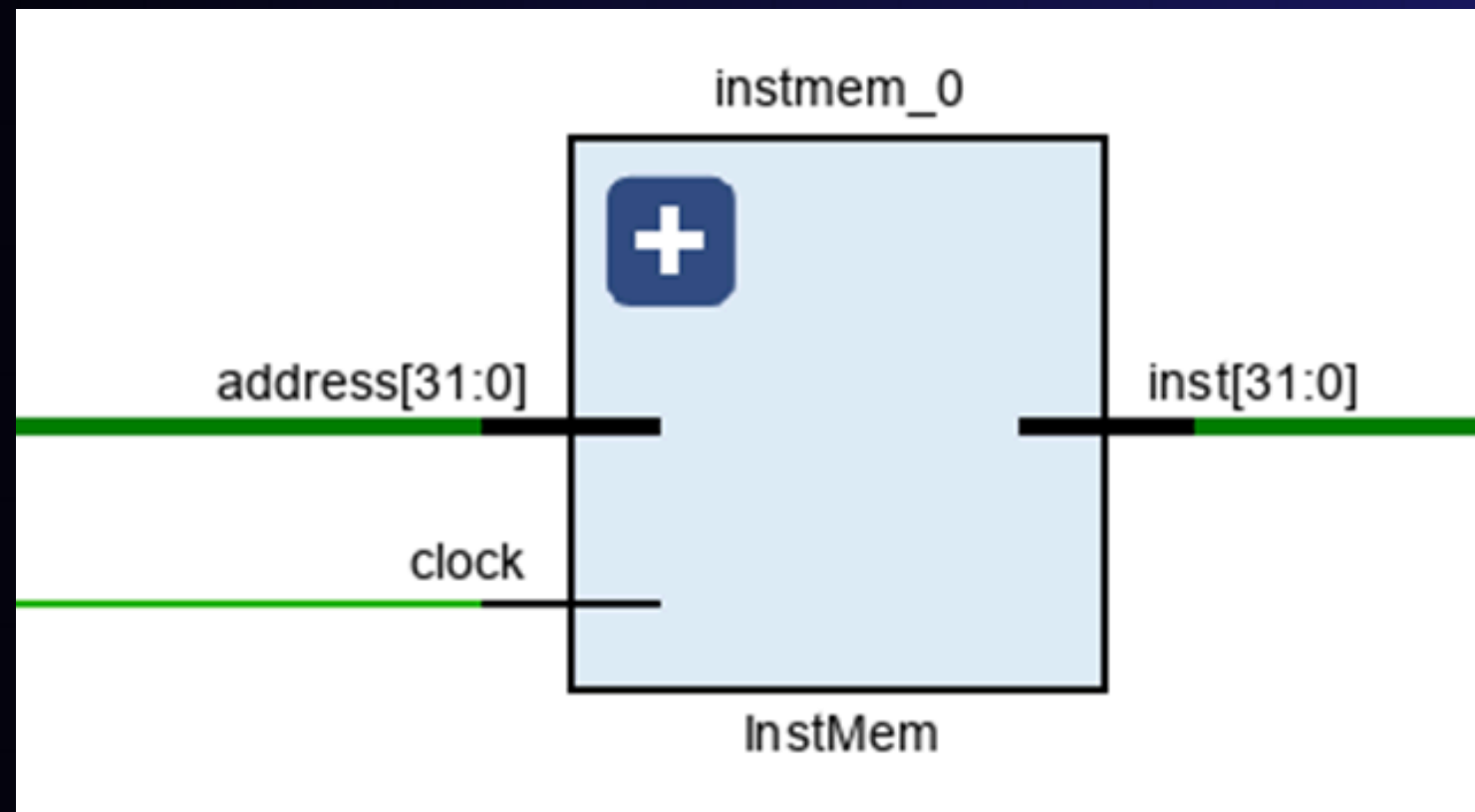

Instruction Memory

 

Data Memory

Phase 2 – DSP Unit Implementation

To implement a 3rd-order moving average FIR filter inside the DSP unit to smooth noisy signals.


How It Works:

For each new input sample $x[n]$, the filter averages it with the previous 3 samples:


$$y[n] = (x[n] + x[n-1] + x[n-2] + x[n-3]) / 4$$

For simplicity, coefficients are all equal and fixed at:

$$b = 1/N = 1/4 = 0.25$$

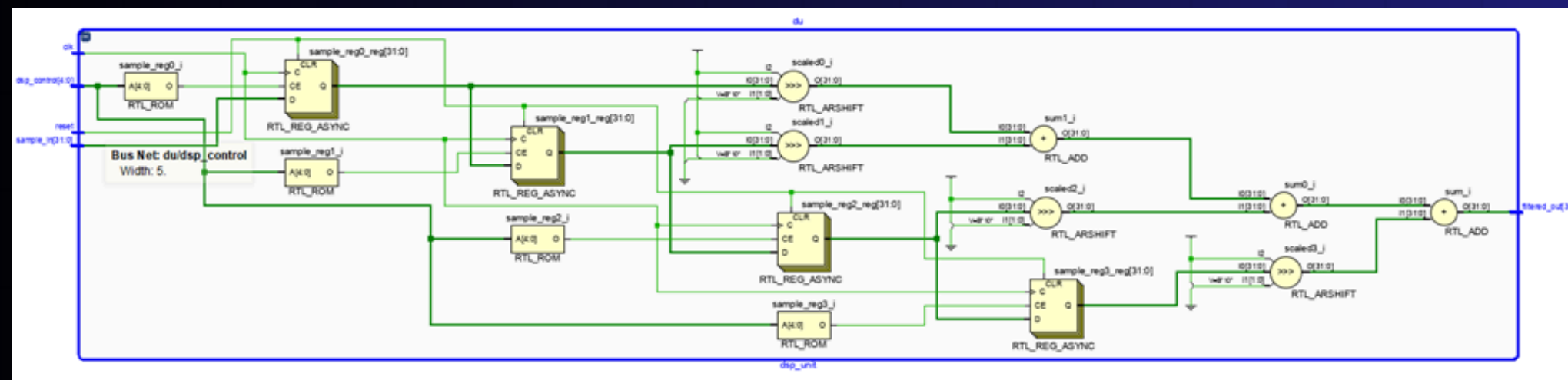

Moving Average FIR Filter RTL Schematic

 

General Diagram for FIR Filters

Phase 3 – Modified Architecture with DSP Unit

1. Modified R-type instruction format:

Old R-type Format:

opcode	rs	rt	rd	shamt	funct
6-bits	5-bits	5-bits	5-bits	5-bits	6-bits

DSP format based on R-type


opcode	rs	rt	rd	dsp	funct
6-bits	5-bits	5-bits	5-bits	5-bits	6-bits

3. Modified Control Unit:

Instruct	Opcode	RegWrit	RegDst	ALUSrc	Branch	DSPorA	MemWr	MemtoR	Op	Jump
R-type	0	1	1	0	0	0	0	0	10	0
lw	100011	1	0	1	0	0	0	1	0	0
sw	101011	0	X	1	0	0	1	X	0	0
beq	100	0	X	0	1	0	0	X	1	0
addi	1000	1	0	1	0	0	0	0	0	0
j	10	0	X	X	X	X	0	X	XX	1
dsp	1	1	1	X	0	1	0	0	11	0

Modified Main Decoder Truth Table

2. Modified Datapath:

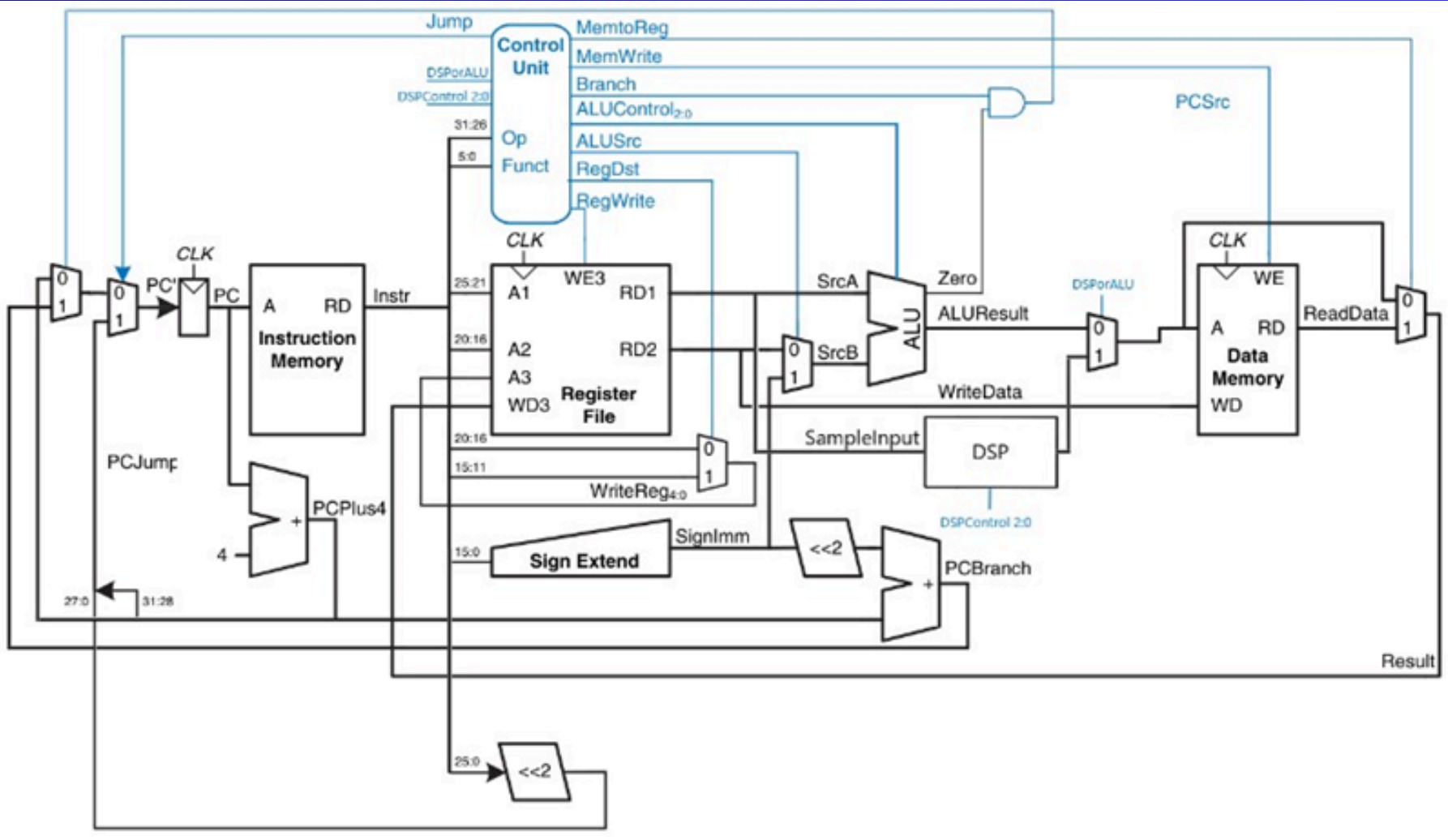

Op	Funct	ALUControl	DSP	DSPControl
0	XXXXXX	010 (add)	XXXXX	XXX
1	XXXXXX	110 (sub)	XXXXX	XXX
10	100000	010 (add)	XXXXX	XXX
10	100010	110 (sub)	XXXXX	XXX
10	100100	000 (and)	XXXXX	XXX
10	100101	001 (or)	XXXXX	XXX
10	101010	111 (slt)	XXXXX	XXX
11	XXXXXX	XXX	1	0

Modified Secondary Decoder Truth Table

Testing:

Testbench Setup:

- Initialized registers with 32 noisy samples
- DSP instruction called for each sample
- Results stored back into registers

Code:

```
20000000 // ADDI $0, $0, 0
```


```
8C040000 // LW $4, 0($0) – Load value from memory address 0 into $4
```

```
8C050004 // LW $5, 4($0) – Load value from memory address 4 into $5
```


```
00853020 // ADD $6, $4, $5 – Add $4 and $5, store in $6
```

```
AC060008 // SW $6, 8($0) – Store $6 into memory address 8
```
 
```
00852022 // SUB $7, $4, $5 – Subtract $5 from $4, store in $7
```




Results:

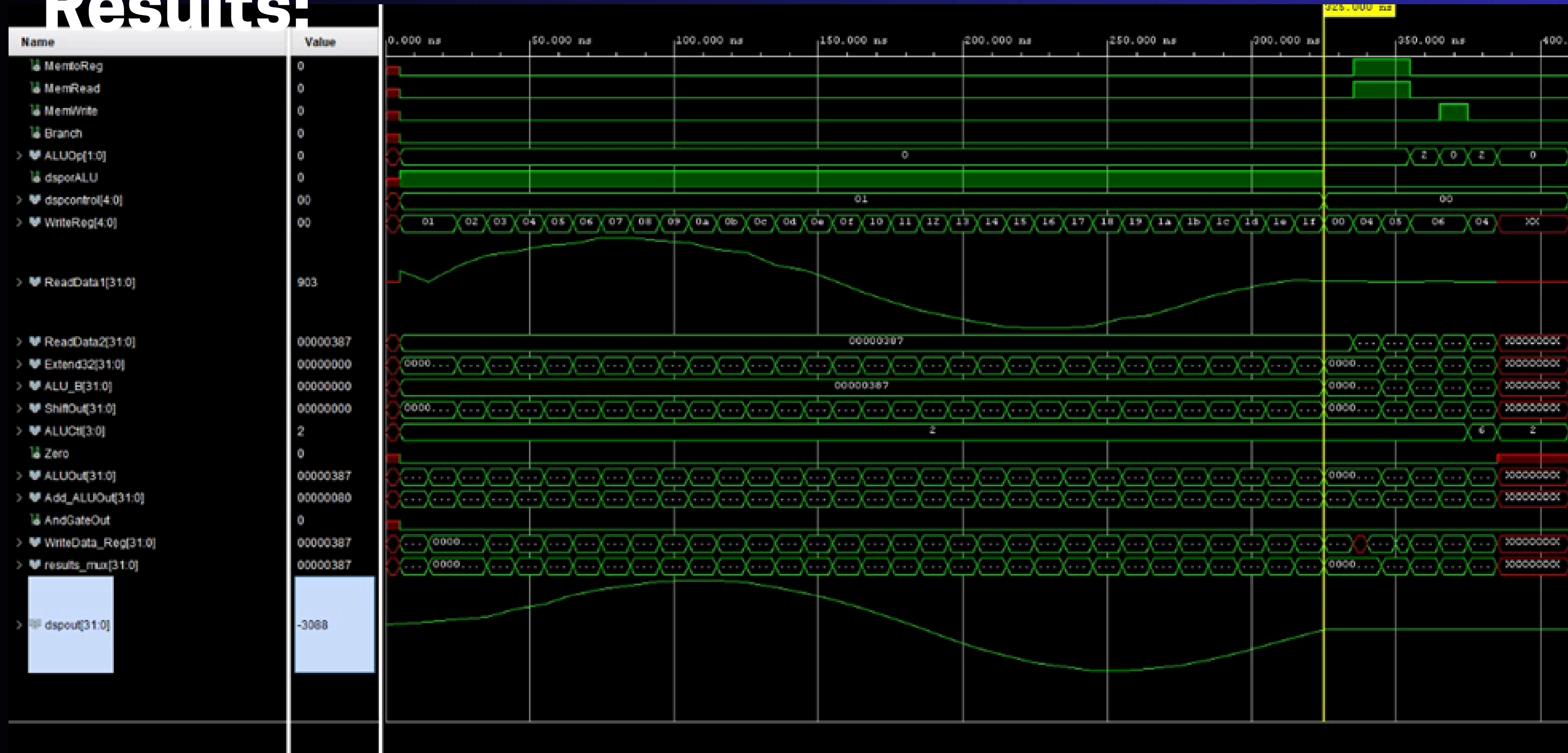

Waveform showing successful the DSP unit

Results:

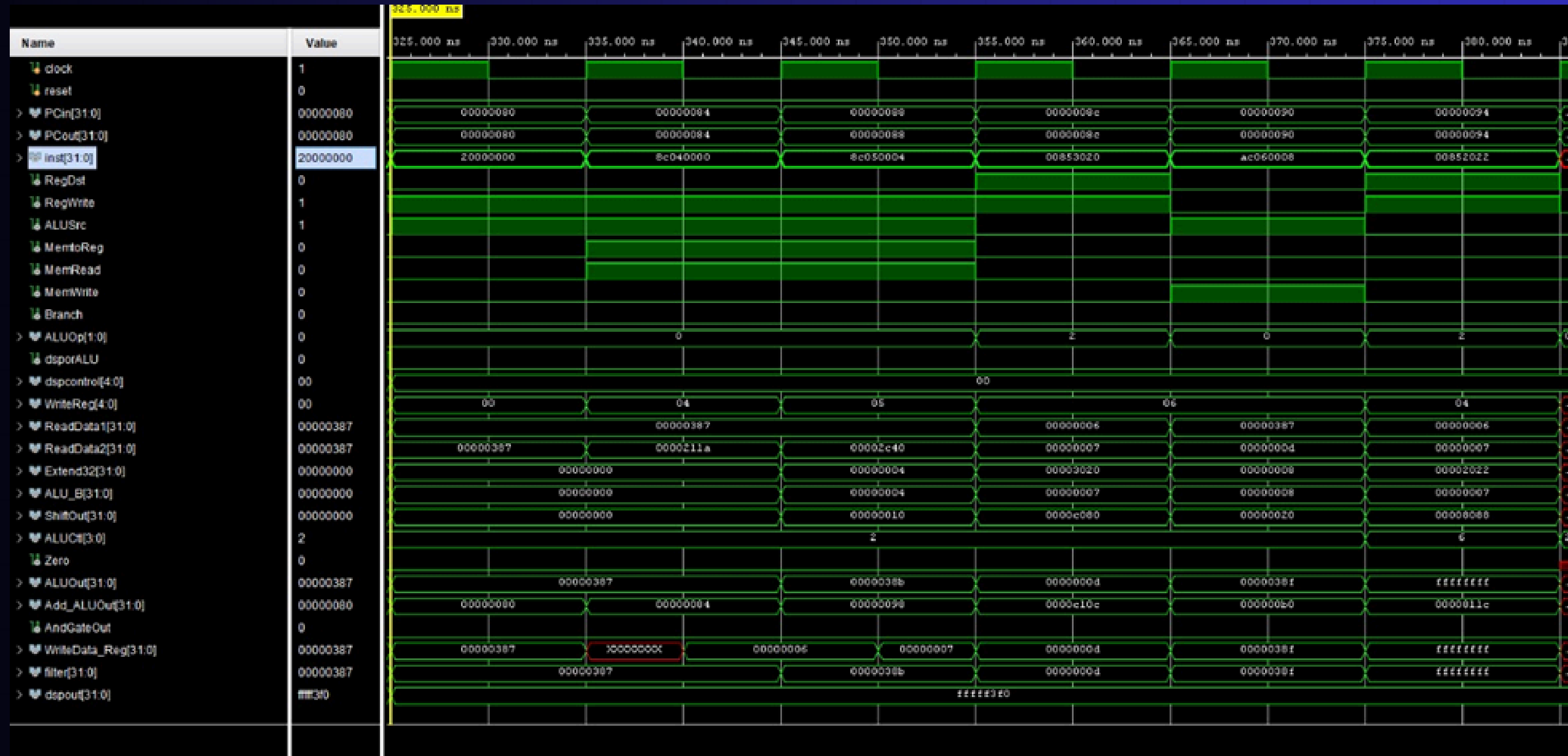

Waveform for multiple R-type I-type Instructions

Results:


Design Timing Summary					
Setup		Hold		Pulse Width	
Worst Negative Slack (WNS): 2.841 ns		Worst Hold Slack (WHS): 0.052 ns		Worst Pulse Width Slack (WPWS): 8.750 ns	
Total Negative Slack (TNS): 0.000 ns		Total Hold Slack (THS): 0.000 ns		Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0		Number of Failing Endpoints: 0	
Total Number of Endpoints: 1014		Total Number of Endpoints: 1014		Total Number of Endpoints: 265	
All user specified timing constraints are met.					

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.



Total On-Chip Power:	0.123 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	26.4°C
Thermal Margin:	58.6°C (5.0 W)
Effective θ_{JA} :	11.5°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Medium

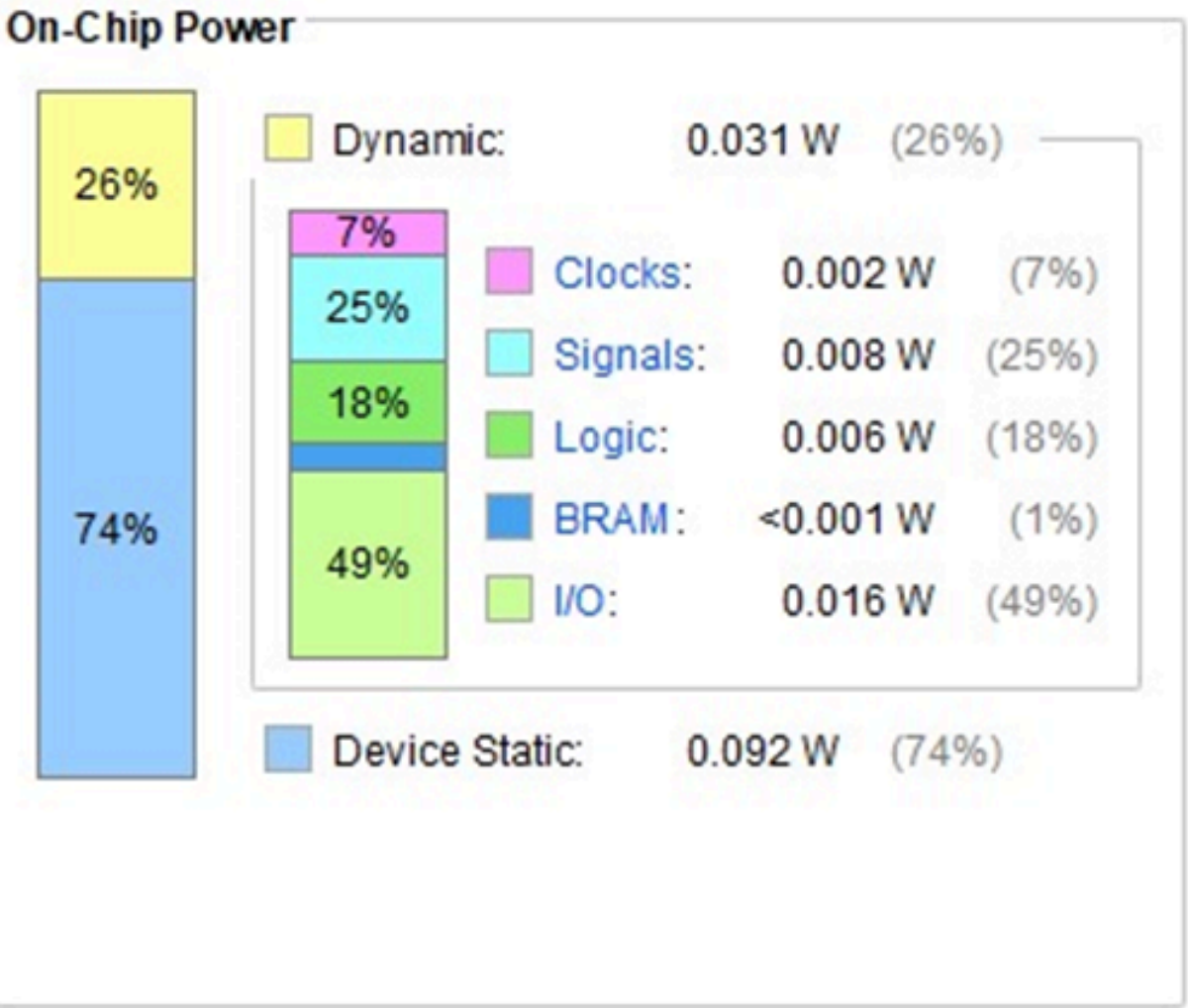[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Synthesis timing report

Synthesis power report

  

THANK YOU

